 


Home work for this Friday

1. Design a 32 bit Adder .
2. Here is D_latch, Dff, JKFF, and 8 divided counter. We set different period clock to get the wave form as following. You can try design the test files to get the wave form.
First, get understand the truth tables.
Then, run the code that we have provided to you.
Finally, try to design your test files(if you have time).

You need to hand in the report next Friday.

1. **D-Latch: Dlatch.vhd**



D	enable	Q	NQ
1/0	1	D	not D

```

library ieee ;
use ieee.std_logic_1164.all;

```

```



entity D_latch is
port( D:          in std_logic;
      enable:       in std_logic;
      Q:          out std_logic;
      NQ:         out std_logic
);
end D_latch;

```

```


architecture behv of D_latch is
begin
  process(D, enable)
  begin
    if (enable='1') then
      Q <= D;
      NQ <= not D;
    end if;
  end process;
end behv;

```

  


2.

D_flip flop: DFF.vhd

 


D	clock	Q	NQ
1/0		D	not D
 
```
library ieee;
use ieee.std_logic_1164.all;
entity DFF is
port( D:          in std_logic;
      clock:       in std_logic;
      Q:          out std_logic;
      NQ:         out std_logic
);
end DFF;
architecture behv of DFF is
begin
  process(D, clock)
  begin
    if (clock='1' and clock'event) then
      Q <= D;
      NQ <= not D;
    end if;
  end process;
end behv;
```



3. J_K flip flop (jkff.vhd)

 

```


library ieee;
use ieee.std_logic_1164.all;
entity JKFF is
port ( clock:      in std_logic;
       J, K:      in std_logic;
       reset:     in std_logic;
       Q, NQ:    out std_logic
);
end JKFF;
architecture behv of JKFF is
signal ss: std_logic;

```


```

begin
process(clock, reset) is
begin
    if (reset='1') then
        ss <= '0';
    elsif (rising_edge(clock)) then
        if(j='1'and k='1')then
            ss <= not ss;
        elsif(j='1'and k='0') then
            ss <= '1';
        elsif(j='0'and k='1') then
            ss <= '0';
        else
            null;
        end if;
    end if;
end process;
Q <= ss;
NQ <= not ss;
end behv;

```

 

4. Divide-by-8 counter: (using 3 J_KFF)

 

```

library ieee;
use ieee.std_logic_1164.all;
use work.jkff;
entity counter8 is
port( clock8: in std_logic;
      reset8: in std_logic;
      Q8:   out std_logic
      );
end counter8;
architecture struct of counter8 is
component JKFF is
port (clock:          in std_logic;
      J, K:          in std_logic;
      reset:         in std_logic;
      Q, NQ:        out std_logic
      );
end component;
signal ss1: std_logic;
signal ss2: std_logic;
begin
Gate1: JKFF port map (clock=>clock8,J=>'1',K=>'1',reset=>reset8,Q=>ss1);
Gate2: JKFF port map (clock=>ss1,J=>'1',K=>'1',reset=>reset8,Q=>ss2);
Gate3: JKFF port map (clock=>ss2,J=>'1',K=>'1',reset=>reset8,Q=>Q8);
end struct;

```

