

## Csc 343 Lab

This is a  $P = A * B$  multiplier. A and B are 4 bit inputs of the multiplier.  
 The design is according to the Laboratory Exercise 6 Figure 6.  
 The components of this multiplier are 12 one-bit adders and 16 AND gates.


one bit adder:

a	b	ci	s	co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$s = a \text{ xor } b \text{ xor } ci$$

$$co = (a \text{ and } b) \text{ or } (a \text{ and } c) \text{ or } (b \text{ and } c)$$

multiplier:

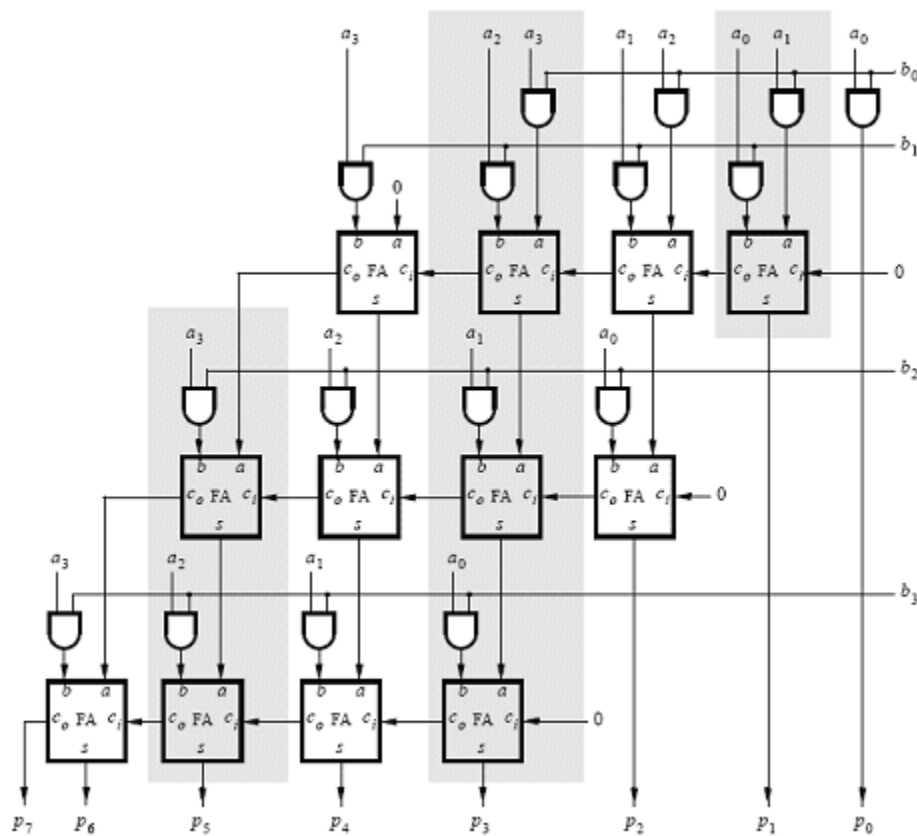

```

=====multiplier.vhd=====
library ieee;
use ieee.std_logic_1164.all;
use work.all;

entity multiplier is

port( A: in std_logic_vector(3 downto 0);
      B: in std_logic_vector(3 downto 0);
      P: out std_logic_vector(7 downto 0)
);

end multiplier;
architecture struct of multiplier is

component adder1 is
port ( a: in std_logic;
      b: in std_logic;
      ci: in std_logic;
      co: out std_logic;
      s: out std_logic
);
end component;

component and1 is
port (x: in std_logic;
      y: in std_logic;
      f: out std_logic
);
end component;

signal ss1: std_logic_vector(7 downto 0);
signal ss2: std_logic_vector(7 downto 0);
signal ss3: std_logic_vector(7 downto 0);
signal ss4: std_logic_vector(3 downto 0);
signal ss5: std_logic_vector(3 downto 0);
signal ss6: std_logic_vector(2 downto 0);

begin

AND_1: and1 port map (x=>B(0), y=>A(0), f=>P(0) );
AND_2: and1 port map (x=>B(0), y=>A(1), f=>ss1(0) );
AND_3: and1 port map(x=>B(0), y=>A(2), f=>ss1(2) );
AND_4: and1 port map(x=>B(0), y=>A(3), f=>ss1(4) );

```

```

AND_5: and1 port map(x=>B(1), y=>A(0), f=>ss1(1) );
AND_6: and1 port map(x=>B(1), y=>A(1), f=>ss1(3) );
AND_7: and1 port map(x=>B(1), y=>A(2), f=>ss1(5) );
AND_8: and1 port map(x=>B(1), y=>A(3), f=>ss1(7) );
AND_9: and1 port map(x=>B(2), y=>A(0), f=>ss2(1) );
AND_10: and1 port map(x=>B(2), y=>A(1), f=>ss2(3) );
AND_11: and1 port map(x=>B(2), y=>A(2), f=>ss2(5) );
AND_12: and1 port map(x=>B(2), y=>A(3), f=>ss2(7) );
AND_13: and1 port map(x=>B(3), y=>A(0), f=>ss3(1));
AND_14: and1 port map(x=>B(3), y=>A(1), f=>ss3(3));
AND_15: and1 port map(x=>B(3), y=>A(2), f=>ss3(5));
AND_16: and1 port map(x=>B(3), y=>A(3), f=>ss3(7));
ADDER_1: adder1 port map (a=>ss1(0), b=>ss1(1), ci=>'0', s=>P(1), co=>ss4(0));
ADDER_2: adder1 port map(a=>ss1(2), b=>ss1(3), ci=>ss4(0), s=>ss2(0), co=>ss4(1) );
ADDER_3: adder1 port map(a=>ss1(4), b=>ss1(5), ci=>ss4(1), s=>ss2(2), co=>ss4(2) );
ADDER_4: adder1 port map(a=>'0', b=>ss1(7), ci=>ss4(2), s=>ss2(4), co=>ss4(3) );
ADDER_5: adder1 port map(a=>ss2(0), b=>ss2(1), ci=>'0', s=>P(2), co=>ss5(0) );
ADDER_6: adder1 port map(a=>ss2(2), b=>ss2(3), ci=>ss5(0), s=>ss3(0), co=>ss5(1) );
ADDER_7: adder1 port map(a=>ss2(4), b=>ss2(5), ci=>ss5(1), s=>ss3(2), co=>ss5(2));
ADDER_8: adder1 port map(a=>ss4(3), b=>ss2(7), ci=>ss5(2), s=>ss3(4), co=>ss5(3));
ADDER_9: adder1 port map(a=>ss3(0), b=>ss3(1), ci=>'0', s=>P(3), co=>ss6(0));
ADDER_10: adder1 port map(a=>ss3(2), b=>ss3(3), ci=>ss6(0), s=>P(4), co=>ss6(1));
ADDER_11: adder1 port map(a=>ss3(4), b=>ss3(5), ci=>ss6(1), s=>P(5), co=>ss6(2));
ADDER_12: adder1 port map(a=>ss5(3), b=>ss3(7), ci=>ss6(2), s=>P(6), co=>P(7) );
end struct;

```

